


ELECTRICITY



Electricity/Electrostatics

Electrostatics is the study of charges at rest

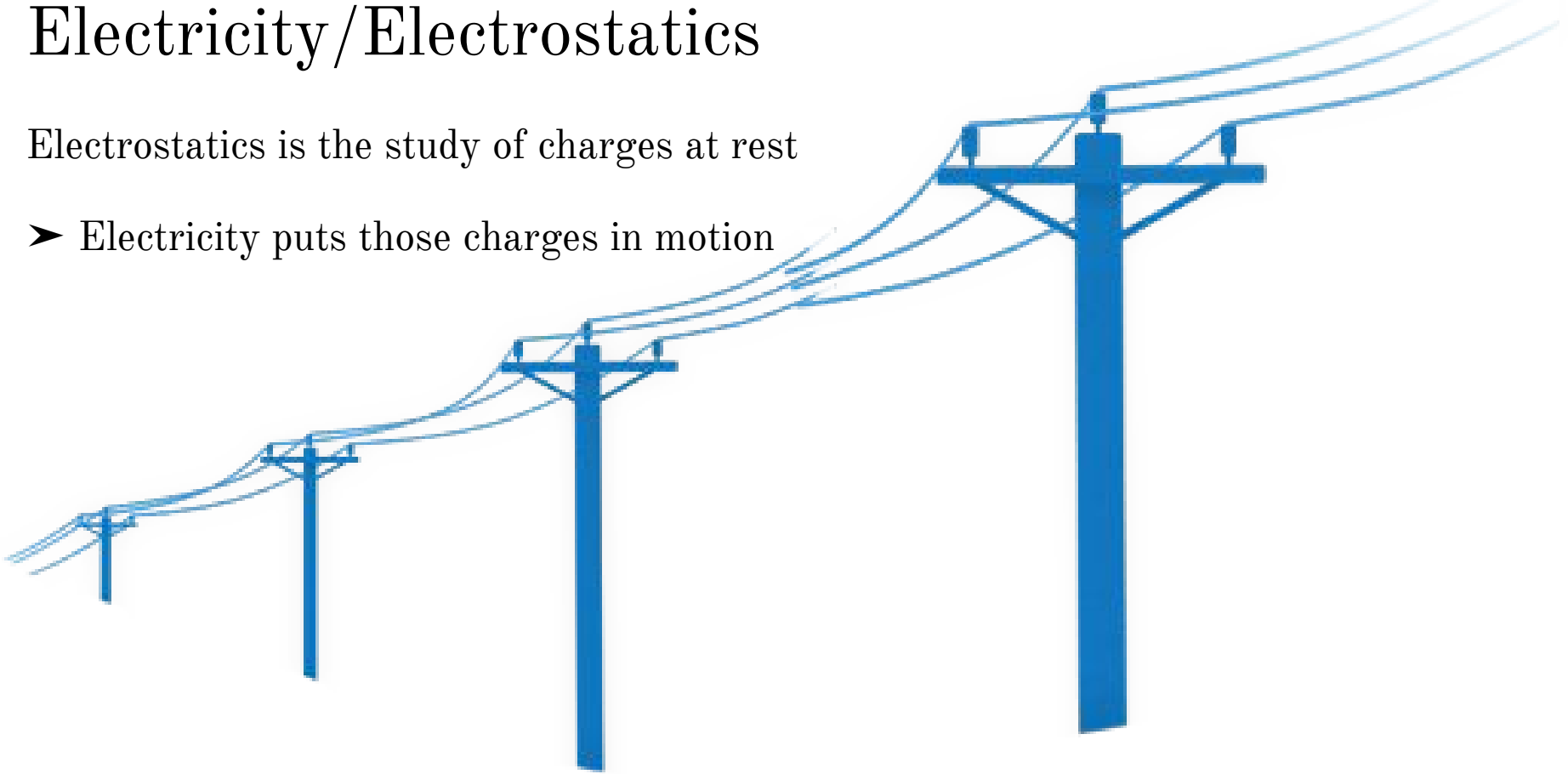➤ Electricity puts those charges in motion




Batteries/Voltage

- Batteries supply electric energy to a system
- Batteries use a chemical reaction to create a potential difference across its positive and negative terminals



Electric Current

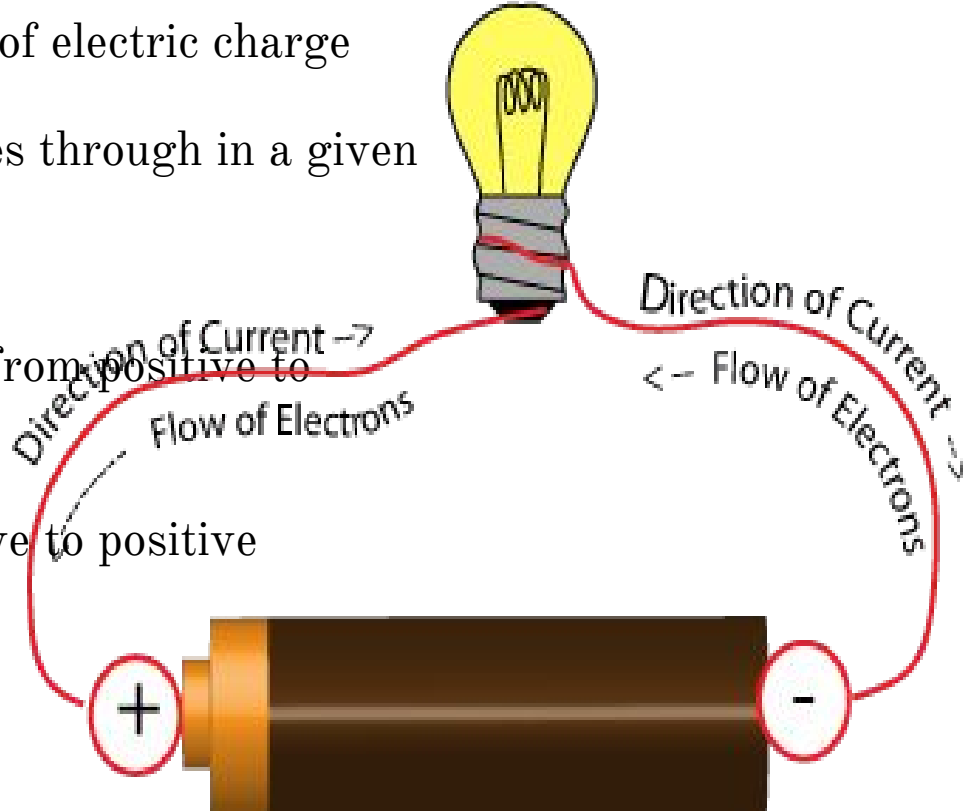- Electric current is the flow of electric charge
- It's how much charge passes through in a given amount of time
- Conventional current runs from positive to negative
- Electrons flow from negative to positive
- $I = \Delta Q / \Delta t$
- Measured in amperes (A)
- $1 \text{ A} = 1 \text{ C/s}$



Ohm's Law

In the early 19th Century, Georg Simon Ohm established through experiments that the current in a wire is proportional to the potential difference applied to its ends


- $V/I = \text{constant}$
- Resistance (R) is measured in ohms (Ω)
- $V = IR$



Resistance

All electronic devices offer resistance to the flow of current

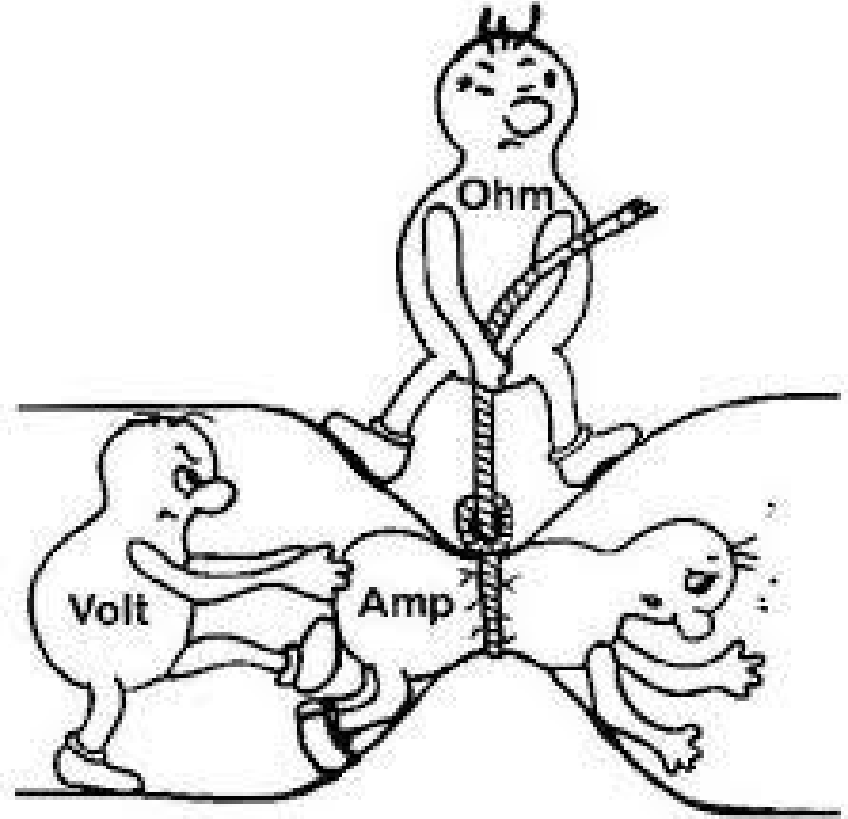- Anything that offers resistance “eats up” electric energy
- It can also be seen as converting electric energy to heat energy
- $R = \rho L / A$
- ρ is the resistivity of the material
- Measured in Ωm



Superconductors and Resistivity

All regular conductors put up some electrical resistance

- The resistivity of a material can depend on temperature, and resistivity usually increases with temperature
- Some materials, once cooled below a particular critical temperature, will offer exactly zero resistance
- Materials acting like this are considered superconductors



Power

Electric energy is useful because it can be easily transformed into other forms of energy

- motors turn it into mechanical work
- electric heaters, stoves, toasters, and hair dryers turn it into thermal energy
- lightbulbs turn it into light and thermal energy
- $P = IV = I^2R = V^2/R$




Series Circuit: Current

When two or more resistors are connected end to end, they are said to be connected in series

➤ Any charge that passes through R1 will also pass through R2 and then R3, etc.

➤ Hence, the same current (I) will pass through each resistor

Measured in Amps (A) or (C/s)

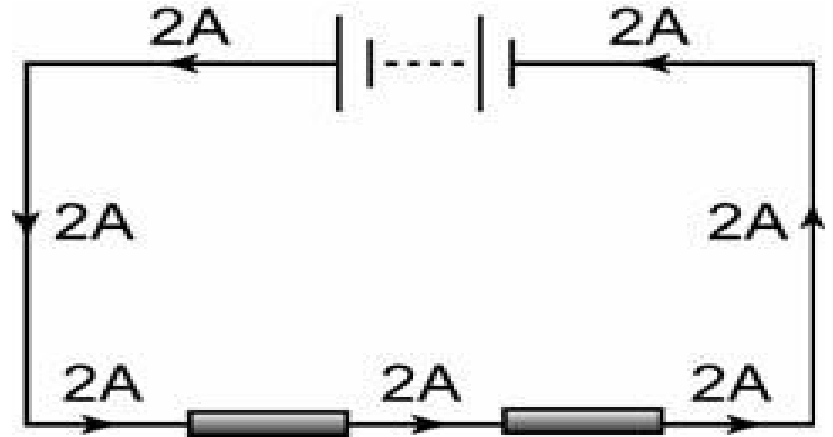

Series Circuits: Voltage

Each resistor eats up some of the energy supplied by the battery

➤ i.e. the voltage will drop across each resistor


➤ Ohm's Law tells us how much the

voltage will drop:

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3, \text{ etc.}$$

➤ $V = V_1 + V_2 + V_3 + V_4$

Measured in Volts (V)

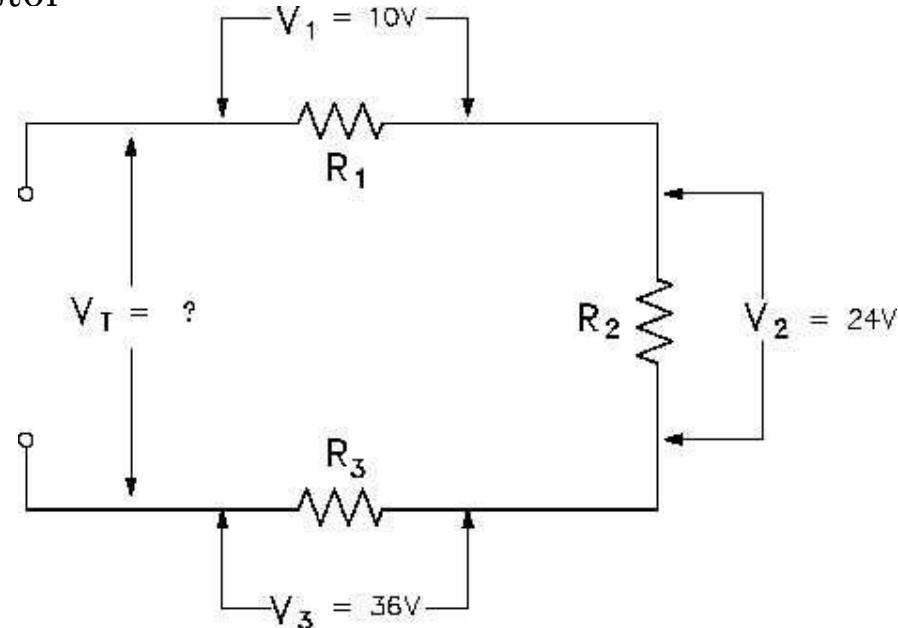

Series Circuits: Resistance

$$V = V_1 + V_2 + V_3 + V_4$$

$$= IR_1 + IR_2 + IR_3 + IR_4$$


The battery doesn't know the difference between one

big resistor and several small resistors working in series

➤ $V = IR_{\text{eq}}$

➤ $R_{\text{eq}} = R_1 + R_2 + R_3 + R_4$

Measured in Ohms (Ω)

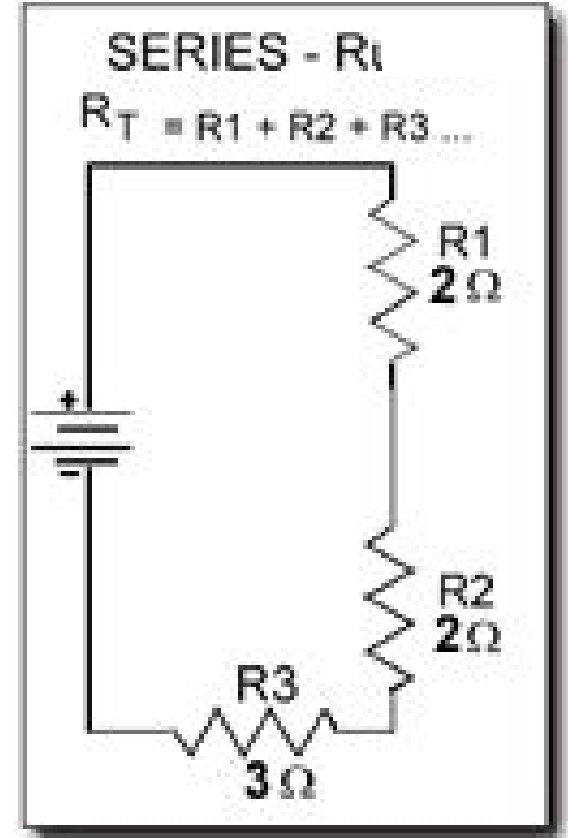

Parallel Circuits: Current / Voltage

Resistors connected in parallel will split the current into separate branches


➤ The “forks in the road” where current can split off into multiple paths are called junctions

➤ $I = I_1 + I_2 + I_3$

Resistors are connected in parallel, each

Experiences the same voltage

- $1/R_T = 1/R_1 + 1/R_2 + 1/R_3$

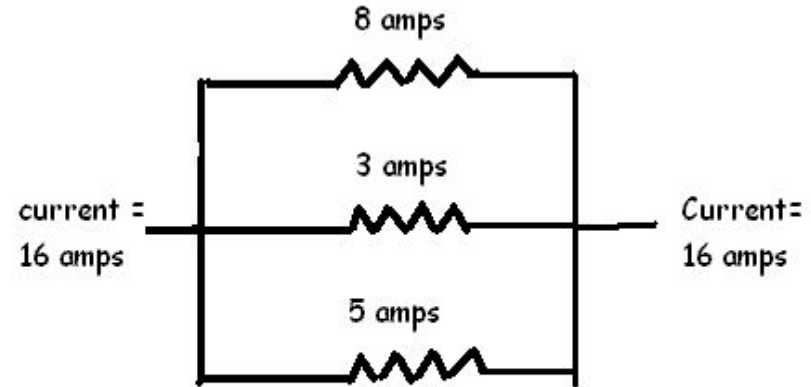

Series/Parallel

	Series	Parallel
V	$V=V_1+V_2+V_3+\dots$	constant
I	Constant	$I=I_1+I_2+I_3+\dots$
R	$R_{eq}=R_1+R_2+R_3+\dots$	$(1/R_T)=(1/R_1)+(1/R_2)+(1/R_3)+\dots$

Kirchhoff's Rules

The rules are really just convenient applications of conservations of charge and energy

1. **Junction Rule:** at any junction, the sum of currents in equals the sum of currents out

➤ (conservation of charge)

Loop Rule: the sum of the changes in potential around any closed path of a circuit must be zero

➤ (conservation of energy)

Capacitors in Circuits

Capacitors in parallel:

- The junction rule tells us that current in equals current out, and by extension, charge in equals charge out
- $Q = Q_1 + Q_2 + Q_3$
- Combine with $Q = CV$
- $C_{eq} = C_1 + C_2 + C_3$

Capacitors in Circuits

Capacitors in series:

➤ Conservation of energy tells us that electric potential supplied by the battery will equal the sum of the potentials used up by circuit components

➤ $V = V_1 + V_2 + V_3$

➤ Combine with $Q = CV$

$(1/C_t) = (1/C) + (1/C_2) + (1/C_3) \leftarrow \text{Series}$



Common Misconceptions

- Batteries do not create or even supply electric charge, all they do is push charge
- Electrical charges move quite slowly (about 1 meter per second), but in a circuit a light bulb will turn on as soon as a switch is turned on because when this happens, charge everywhere in the circuit begins to move.
- Charge does not become used up as it flows through a circuit, and the amount of charge that comes out of a light bulb is the same amount that enters the light bulb.

Question (Sanity Check)

A hair dryer draws 9.0 A when plugged into a 120-V line

a) What is its resistance?

b) How much charge passes through in 15 min?

