




Everything you need to know about Electricity

By Jason Brown and Charlie Reynolds


$$I = Q/t$$

Current Measures the flow of electrons and is calculated by dividing the change in charge by the change in time. It is measured in Amperes(coulombs per second).



Common Misconception-Batteries

Current in a circuit does not flow from the negative to positive terminals of battery .

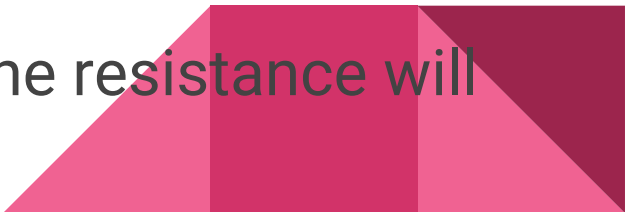- Rather a conventional flow of current in a circuit flows from **Positive to Negative**
 - Batteries supply this electrical energy by converting stored chemical energy
 - **Also**, if voltage is changed in a battery the resistance will remain the same
- 


$$R = \rho l/A$$

Resistivity is the quantity that determines how much energy it takes to push charge through a wire. Resistivity is measured in Ω (Ohms).



Ohm's Law

Resistance dictates flow of current

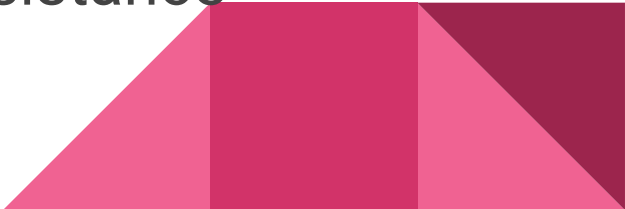- $V=IR$
 - Resistance measured in Ohms Ω
 - Voltage is the energy lost across a section of a circuit
 - it depends on the current and the resistance
- 

Power and Work

$$P=VI = V^2 /R = I^2 R$$

- Energy per time measured in watts
- (found by substitution)

$$W = qV$$

- Work measures energy
- Charge times Voltage (energy per charge).

$$P = W/t$$



Circuits: Series


Resistors connected end to end are in SERIES

- Each resistor eats up energy creating a Voltage drop
 - Resistance Total= Sum of all the Resistors
- Current is constant
- Voltage Total= Sum of the Voltages across all resistors



Circuits: Parallel

Junctions split current into multiple parallel paths

- Voltage drop is equal across all legs of a parallel circuit.
 - Current varies depending on resistance.
 - The resistance of a parallel circuit is less than either of the separate paths.
- 

Kirchoff's Rules

1. Junction Rule -- Current into a junction will equal current out of the junction
2. Loop Rule -- sum of potential charges in a loop is zero



Capacitors in Circuits/ Series


- Potential supplied by battery
 - Q/C total = The sum of each capacitors reciprocal
- **Common Mistake:** Remember that capacitors in series to take the reciprocal of the sum



Common Mistake-- Capacitors vs Resistors

In a series circuit, add resistance and take the reciprocal of capacitance.

In a parallel circuit, add capacitance and take the reciprocal of resistance.



Example Problem (for us)

A circuit has 4 resistors connected in series, all of which have a resistance of $10.0\ \Omega$. If $4.00\ \text{A}$ of current flow through the circuit how much work is done by the battery in one minute.

Answer: $W = 38400\text{J}$



Problem to do on your own

If a circuit has 5 resistors connected in parallel, each of which has 10.0Ω of resistance, and 8.00 A of current flow through the circuit from two batteries of equal strength, what is the power of each battery.

Answer: $P = 64 \text{ w}$

