

The image features two hands, palms facing each other, holding a glowing, spherical orb of electricity. The orb is composed of numerous bright, branching lightning bolts that radiate outwards, creating a complex, web-like pattern of light. The hands are positioned on either side of the orb, with fingers slightly spread. The background is a solid, dark black, which makes the bright light of the electricity stand out prominently. The word "Electricity" is written in a bold, dark blue font across the center of the glowing orb. Below the word, there are three small white dots arranged horizontally. At the bottom of the image, the names of the group members and their period are listed in a white, serif font. In the bottom right corner, the website "onedio.com" is written in a small, white, sans-serif font.

Electricity

...

Lily, Laura, Lynette, Elyse, Gillian, Emma, Hailey
Period 2

Electrostatics vs. Electricity

- ***Electrostatics*** is the study of charges at rest
 - Electrostatics: to help remember the difference the word static means stationary or not moving
- ***Electricity*** puts those charges in motion

Electric Current

- Defined as the flow of electric charge over a period of time
 - $I = \Delta Q / \Delta t$
- Measured in Amperes, A
- Is a completely dependent variable - it relies on voltage and resistance

Batteries

- Supply electric current to a system
- **They only *push* charge**
- They do NOT create or supply electric charge
- Use a chemical reaction to create a potential difference (voltage).

Ohm's Law

- Current in a wire is proportional to potential difference (voltage) applied to its ends
- **V=IR**
 - Voltage: volts (V)
 - Current: amps (A)
 - Resistance: ohms (Ω)
- Resistance and voltage are **independent**
- Current is **dependent**


Resistivity

- All electronic devices offer resistance to the flow of current
- *Resistivity* is a measure of the resisting power of a specified material to the flow of an electric current
- $R = \rho L/A$
- ρ (greek letter rho) = the resistivity of a material
- Measured in Ωm = Ohm meters
- *Resistivity* depends on temperature
 - **Hot** temperature → **increased** resistivity
 - **Cold** temperature → **decreased** resistivity

Power

- Electric energy can be easily transformed into other forms of energy
 - Examples:
 - Lightbulbs turn it into light energy and thermal energy
 - Motors turn it into mechanical work
 - Electric heaters, stoves, and toasters turn it into thermal energy
- $P = IV = I^2R = V^2/R$

Series Circuits

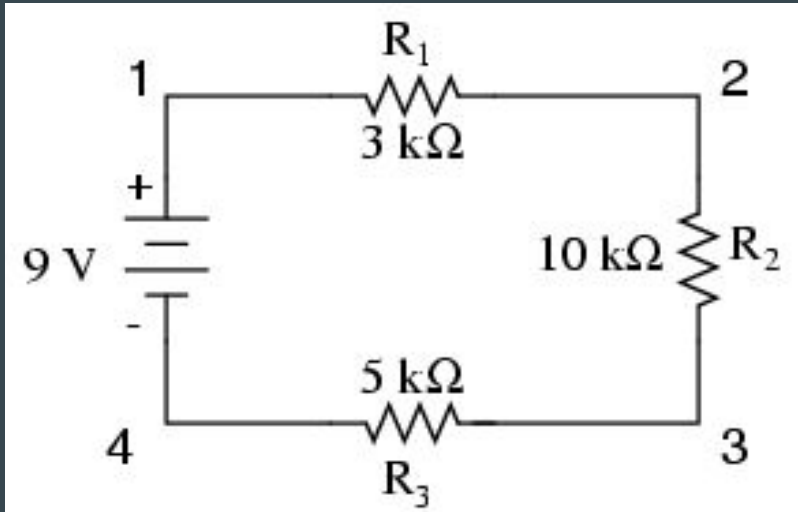

- **Series:** two or more resistors are connected end to end
- **Voltage will drop across each resistor**
- Same current will pass through each resistor
- Battery doesn't know difference between one big resistor and several small resistors working together


$$V = V_1 + V_2 + V_3 + \dots$$

$$I = \text{constant}$$

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots$$

Parallel Circuits

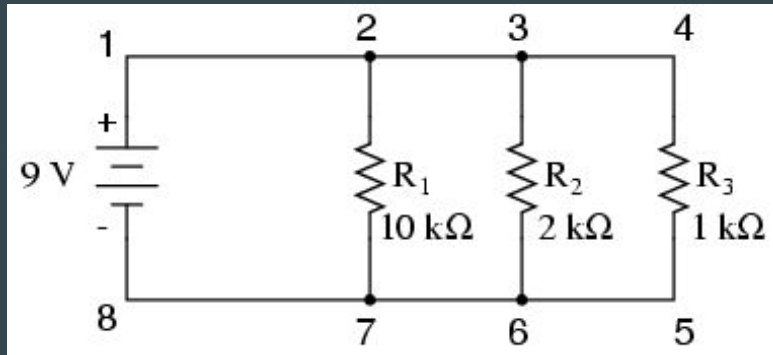- Resistors connected in parallel will split the current into branches that run parallel to each other
- Junctions are the joints where these branches connect
- Voltage remains constant across the circuit
- Current is split between each individual branch
- Resistance is simply the reciprocal of a series circuit



$$V = \text{constant}$$

$$I = I_1 + I_2 + I_3 + \dots$$

.

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Kirchhoff's Rules

1. **Junction Rule:** at any junction, the sum of currents in equals the sum of currents out (conservation of charge)
2. **Loop Rule:** the sum of the changes in potential around any closed path of a circuit must be zero (conservation of energy)
 - These rules are used to find values in circuits that are not all parallel or all series, but mixed

Capacitors in Circuits

- Capacitors in *parallel*:

- $Q = Q_1 + Q_2 + Q_3$

- $C_{eq} = C_1 + C_2 + C_3$

- Capacitors in *series*:

- $V = V_1 + V_2 + V_3$

- $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$



Common Mistake #1

- $V=IR$
- Do not forget that CURRENT is the DEPENDENT variable and voltage is INDEPENDENT

- To avoid this common mistake rewrite the equation as
 - $I=V/R$
 - This way you remember current is the DEPENDENT variable

Common Mistake #2

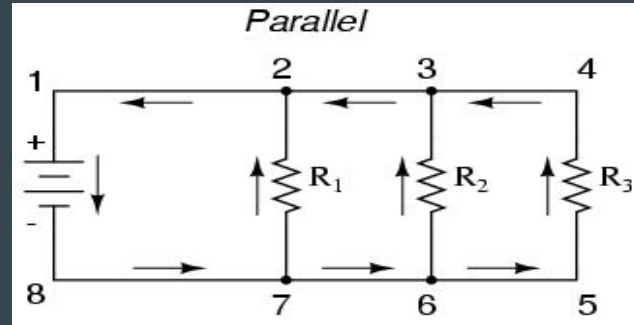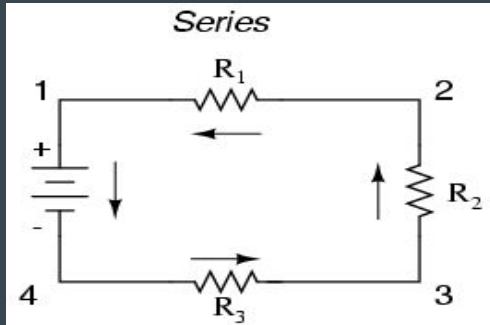- Know how to identify a SERIES and a PARALLEL circuit



- To avoid this common mistake know that a series circuit follows in a single loop with no junctions and a parallel circuit has various pathways for the current to travel on

Common Mistake #3

- Do not mix up the rules for Series and Parallel

- Parallel

$$V = \text{constant}$$

$$I = I_1 + I_2 + I_3 + \dots$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

- Series


$$V = V_1 + V_2 + V_3 + \dots$$

$$I = \text{constant}$$

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots$$

Common Mistake #4

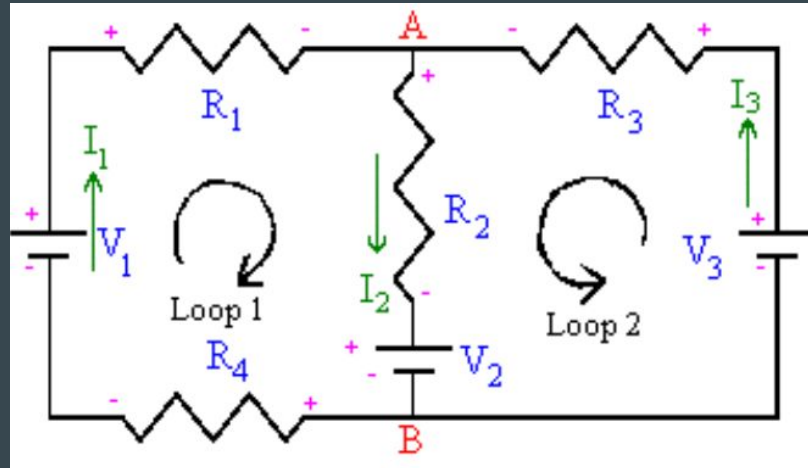- Do not forget that when current is moving AGAINST the flow you ADD resistors and SUBTRACT for BATTERIES
- Normally when the current runs from the battery to a resistor you SUBTRACT when you reach the RESISTOR
 - However, SUBTRACTION switches to ADDITION when the current runs against the system.



Common Mistake #5

- Batteries only push charge
- It is commonly mistaken that batteries supply and store charge
- How to avoid: remember that capacitors are the ones that store charge and charges are supplied in wires

Common Mistake #6

- Do not mix up resistance and resistivity
- $R = \rho L/A$
 - R is resistance
 - ρ is resistivity
- Avoid this common mistake by remembering you have to use the resistivity(ρ) to find the resistance(R)

Kahoot

Ω